

General License Course



Chapter 4.5

Active Components



ARRL *The national association for*
AMATEUR RADIO

Atomic Structure

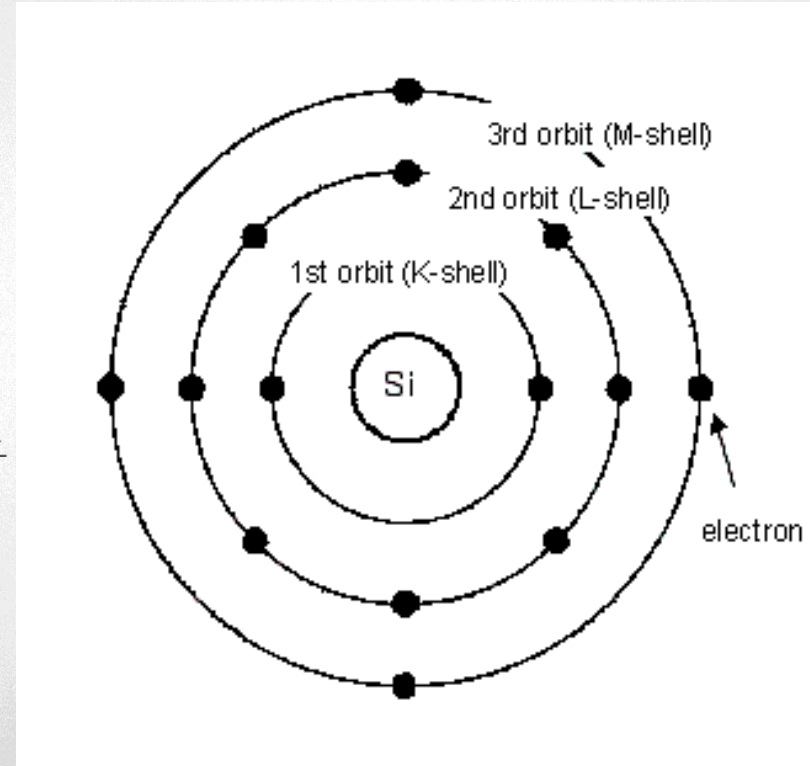
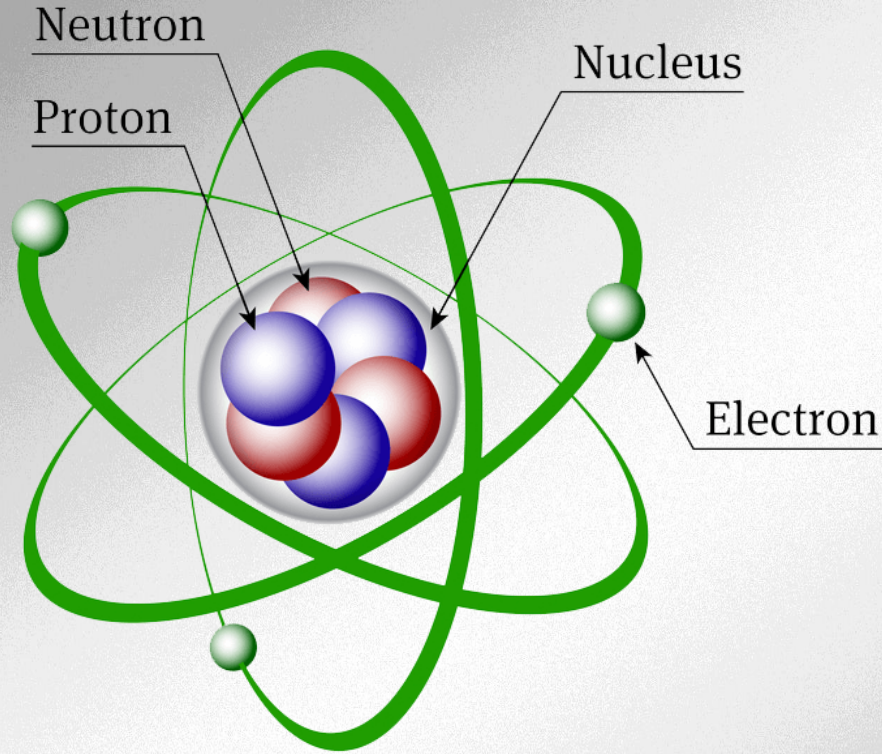


The number of Protons = the number of Electrons

Atomic Lattice

Germanium and Silicon are used in semiconductor devices.
Each has 4 electrons in their outermost valence electron shell



Covalent Bonding

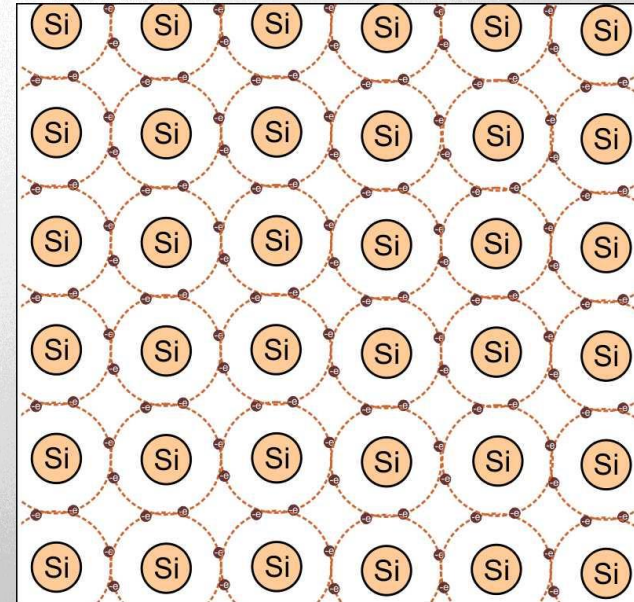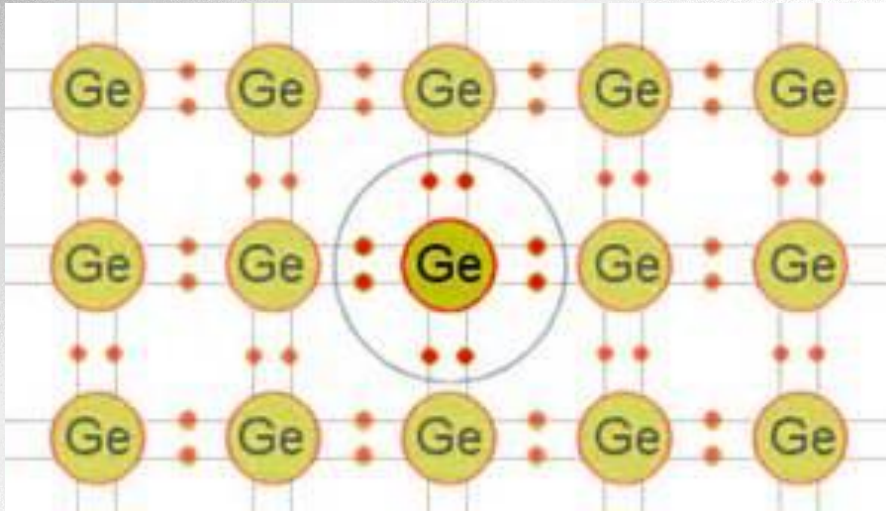

ARRL The national association for
AMATEUR RADIO

Semiconductor

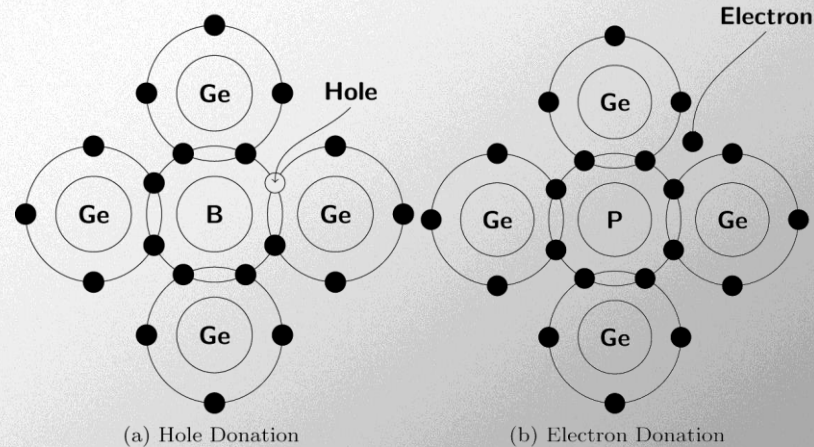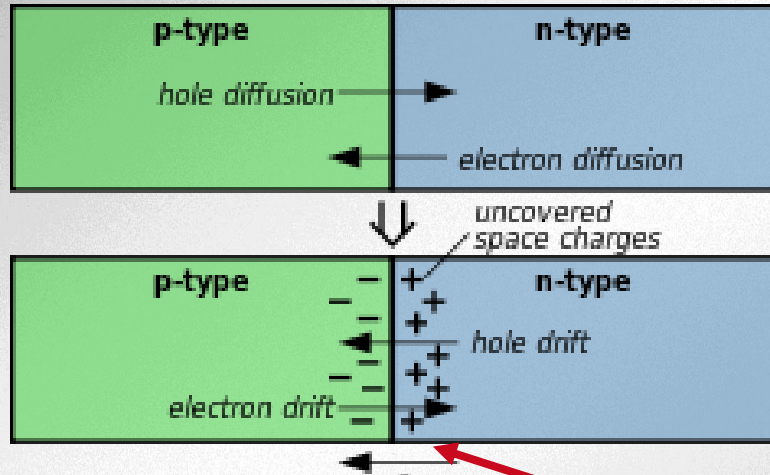Semiconductor material is created by “doping” crystalline (non-conducting) lattices with impurities to allow them to “semi-conduct”



Near the PN junction, electrons diffuse across to combine with holes, creating a "depletion region"





ARRL The national association for
AMATEUR RADIO

Semiconductor Components

- Diodes & Rectifiers
- Junction diode - PN semiconductor junction blocks flow of current in one direction
- Current flows when (+) voltage is applied to the P-type material and (-) voltage to the N-type material - **forward bias**

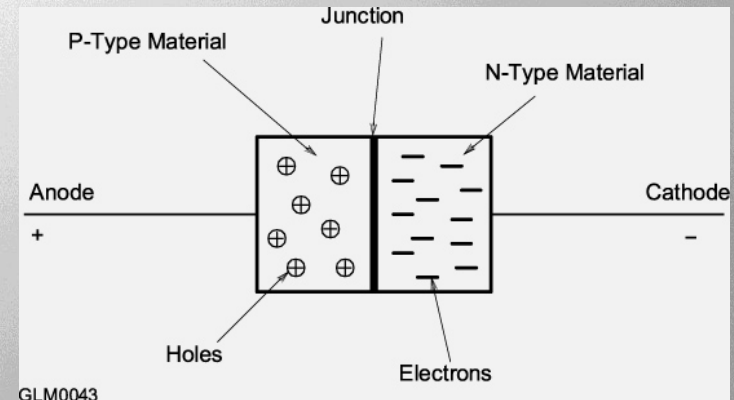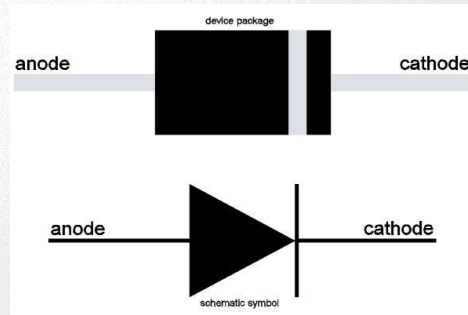Diode forward voltage drop (or *junction threshold voltage*, to overcome the depletion region) : **germanium 0.3 V - silicon 0.7 V**




Bipolar Transistors

- Bipolar junction transistors have 3 electrodes:
 - Collector (C)
 - Base (B)
 - Emitter (E)
- Emitter-Collector current flow is controlled by the much smaller current flow between base and emitter




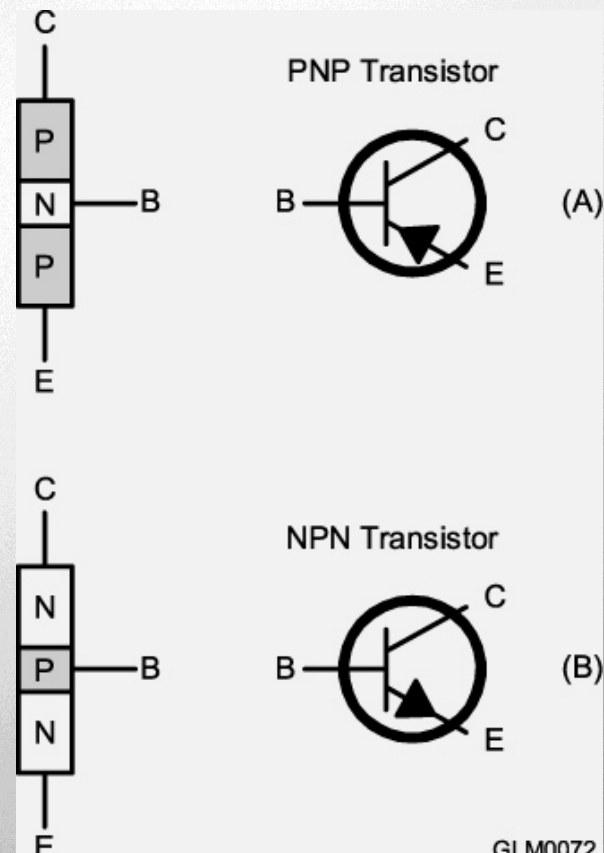ARRL The national association for
AMATEUR RADIO



Bipolar Transistors

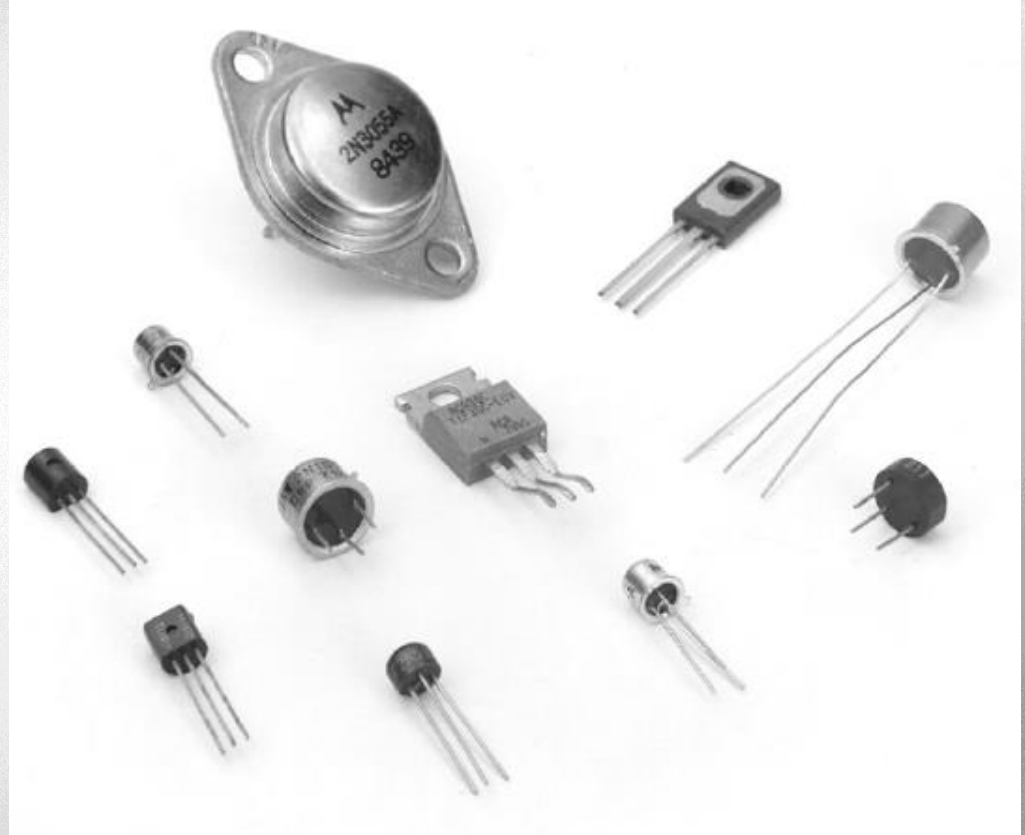- Very little base-emitter current is required for emitter-collector current to flow
- Control of the above larger current by a smaller current is *current gain* or *beta* (β)



ARRL The national association for
AMATEUR RADIO

Bipolar Transistors


- Transistors can be used as as *switches* for voltage and current
- *Saturation* – when further increases in input result in no output change (logic HI or 1)
- *Cutoff* – when the input signal reduces output current to zero (logic LO or \emptyset)
- Saturation & cutoff regions can represent *digital ON/OFF or 1/ \emptyset values* - Stable Operating Points for logic circuit use

Field Effect Transistor (FET)



The FET has 3 electrodes; Drain (D), Source (S) and Gate (G)

Current flow is controlled by the voltage between gate and source.

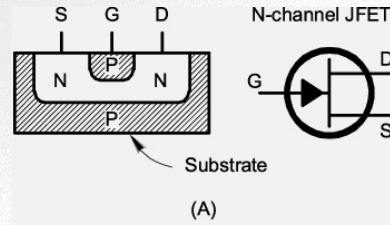Metal-Oxide-Semiconductor FETs (MOSFETs) insulate the gate from the channel with a thin layer of oxide



Junction FET
or JFET

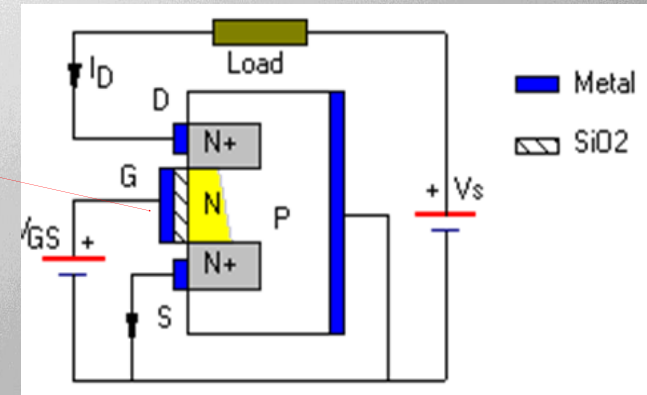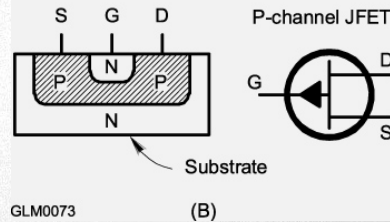


(Static Sensitive!)



ARRL The national association for
AMATEUR RADIO


Vacuum Tubes

- Tube terminology:
 - *Filament or heater* – heats the cathode to allow it emit electrons
 - *Cathode* – source of electrons (negative bias)
 - *Control grid* – regulates electron travel between the cathode and plate
 - *Screen grid* – reduces grid-to-plate capacitance
 - *Suppressor grid* – prevents electrons from traveling between the plate and control/screen grids
 - *Plate* – collects electrons

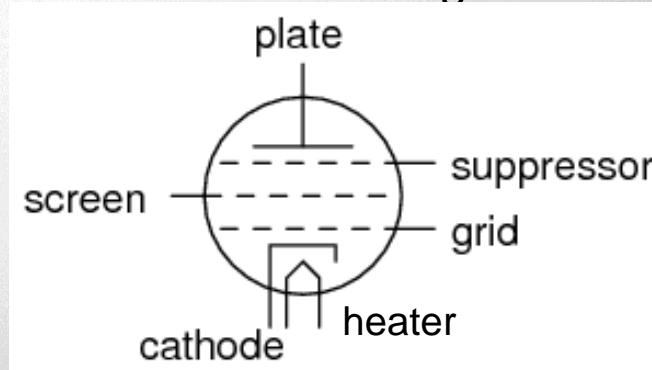

ARRL The national association for
AMATEUR RADIO

Pentode Cross-Section

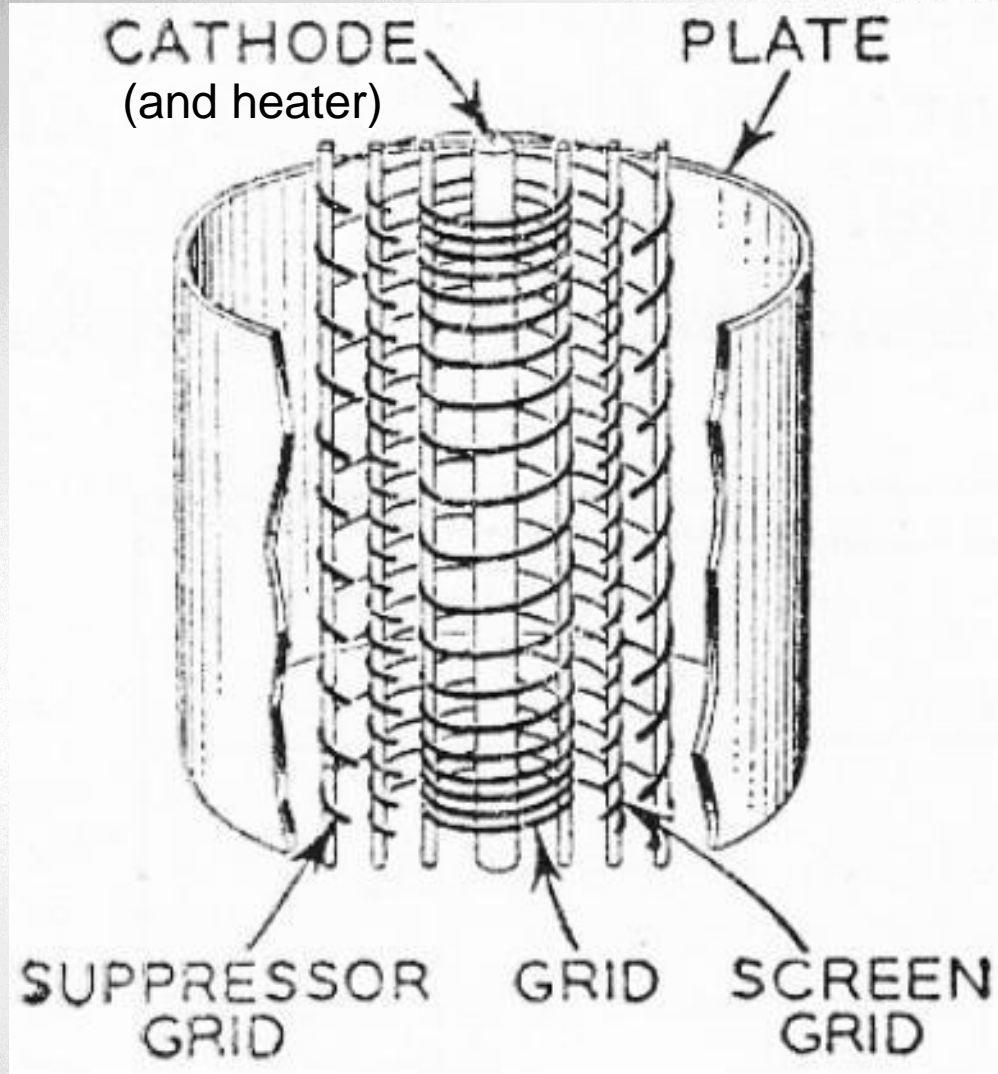

ARRL The national association for
AMATEUR RADIO

Vacuum Tubes

- All *amplifying* tubes have at least 3 electrodes
- Compared to transistors, the tube is most like the field effect transistor (FET)
- Vacuum tubes sometimes operate at *hazardous voltages* as high as 2000 to 3000 volts (use **CAUTION!**)






ARRL The national association for
AMATEUR RADIO



Analog Integrated Circuits (ICs)

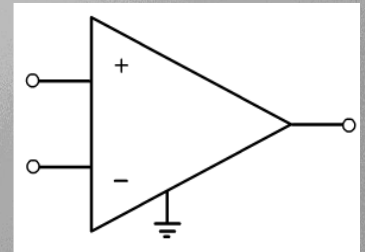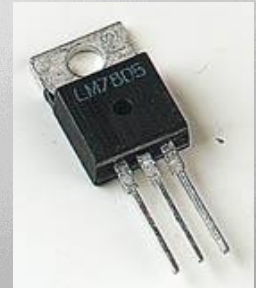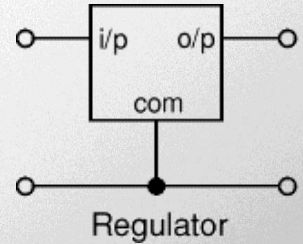- **Analog ICs** or “chips”:
- Can have an output value anywhere between zero volts and the supply voltage
- Used for amplification, filtering, measurement, and power control
- A linear voltage regulator is used to maintain a power supply output at a constant voltage over a wide range of currents (*Analog*)
- Operational amplifiers (op amps) are used for dc and audio circuits (*Analog*)



ARRL The national association for
AMATEUR RADIO

Digital Integrated Circuits (ICs)

- Digital ICs operate with discrete values of voltage and current which can easily represent the binary numbers system (logic) values 0 and 1 (lo, hi)
- Digital electronic circuits operate with only two stable states of operation, ON or OFF (see above)
- Digital circuits can perform computations or control functions
- CMOS (complementary-symmetry metal-oxide semiconductor) technology is popular because of its high speed and low power consumption (vs. TTL) - *often Static Sensitive!*




Digital Logic Basics

- The basic building blocks of digital circuits are called *gates*
 - *Inversion* (changing a 1 to a 0 and vice versa)
 - OR and AND functions
 - Inverted versions are NOR and NAND
 - Truth tables explain the functions implemented by the gates


Digital Logic Basics

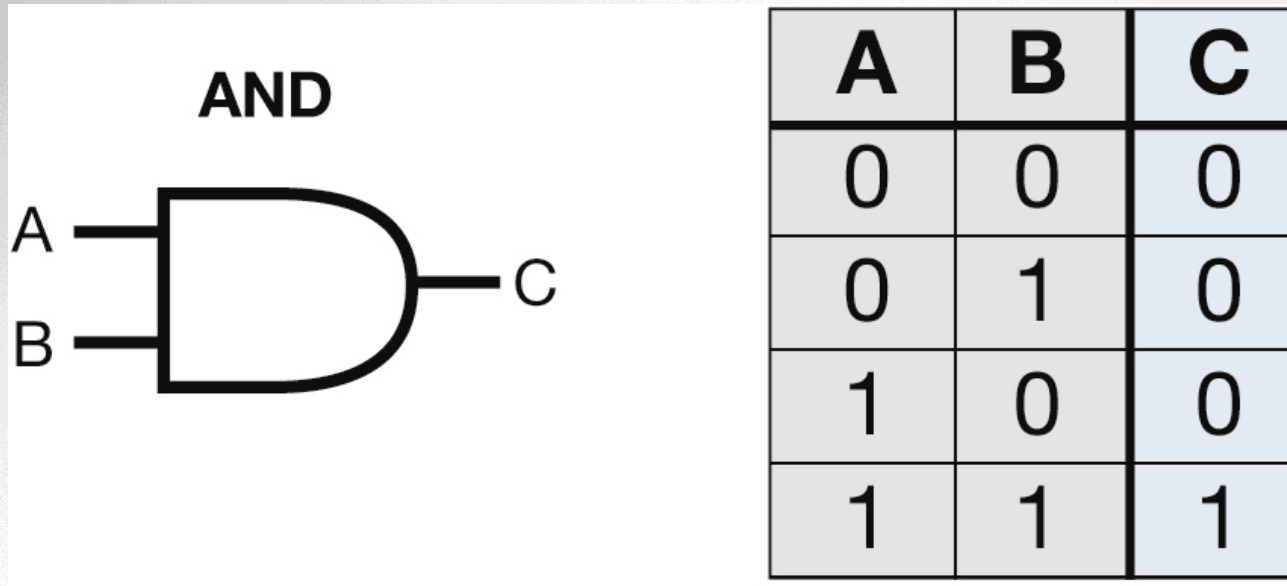For a two input AND gate, the output is high only when both inputs are high




Digital Logic Basics

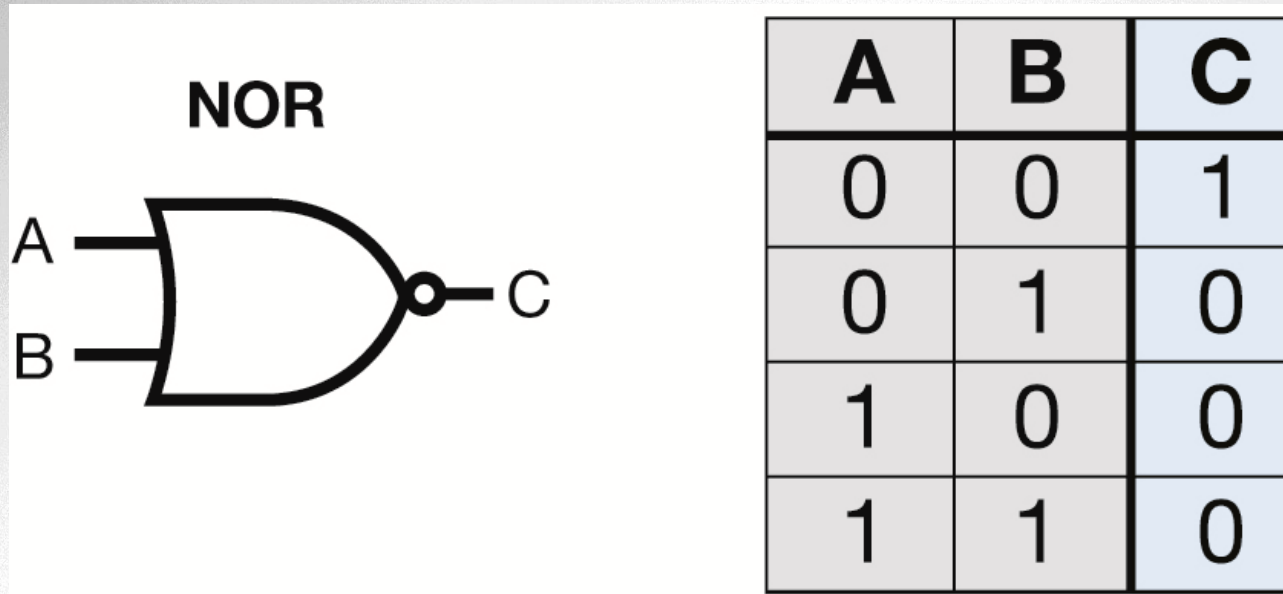For a two input NOR gate, the output is low when either or both inputs are high.



Digital Logic Basics

- Flip-flop – has 2 stable output states (Hi, Lo) - when pulsed by the clock output O changes to whatever logic level is present at input D
- Sequential logic – built on flip-flops feeding other flip-flops (used in counters)
- Examples : A 3-bit counter (one with 3 flip-flops) can count $2^3 = 8$ different states - a 4-bit counter (one with 4 flip-flops, shown below) can count $2^4 = 16$ different states
- Shift register – a clocked array of circuits that passes data in steps along the array

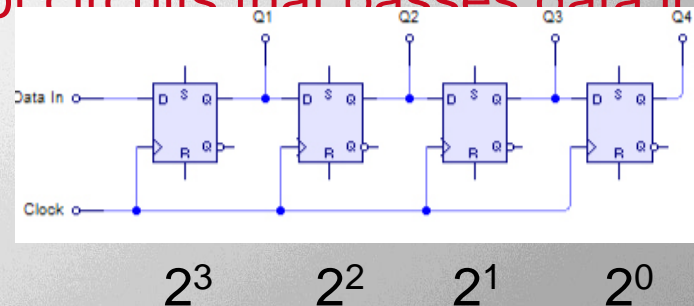

RF Integrated Circuits

- RF ICs are designed for functions commonly used for *radio frequencies*
- Low-level high-gain amplifiers
- Mixers
- Modulators and demodulators
- Filters
- **MMIC** (monolithic microwave integrated circuit) - designed to work through microwave frequencies



ARRL The national association for
AMATEUR RADIO

Microprocessors & Components

- A microprocessor (AKA microcontroller) is a computer on a single Integrated Circuit
- Capable of performing billions of instructions per second using combinations of digital logic gates
- Has parallel and serial input-output ports, counters and timers
- Most are built from CMOS logic components
- A microprocessor can replace complex digital circuitry



ARRL The national association for
AMATEUR RADIO



Microprocessor Components

- Memory:
- Volatile memory loses the data stored when power is removed
- Nonvolatile memory retains data permanently even when power is off
- Random-access memory (RAM) can be read or written to in any order
- Read-only memory (ROM) stores data permanently and can't be changed




Microprocessor Components

- Interfaces:
- Serial interface transfers one bit of data in each operation
- Parallel interface transfers multiple bits of data in each operation
- RS-232 serial interface has been replaced by USB (universal serial bus) serial interface
- Modern computers don't have RS-232 ports; you may need to use a USB to RS-232 converter to interface with your transceiver



Microprocessor Components

- Visual Interfaces:
- *Indicator* – device that presents ON/OFF information (LED)
- *Display* – device capable of presenting text or graphics in visual form
- An LED is a special diode that produces light when it is forward biased
- LEDs are available in several different colors, including white
- LEDs are replacing *incandescent* light bulbs because they last longer, react faster, and consume less power.

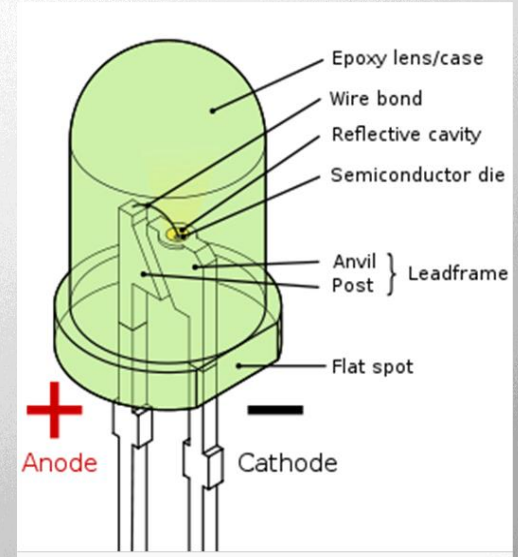

Microprocessor Components

- *Liquid crystal display* (LCD) – created by sandwiching liquid crystal material between transparent glass panels
 - When voltage is applied to the electrodes on the front panel, the liquid crystals twist and turn the segment from light to dark-colored
 - LCDs require ambient or back lighting since the liquid crystal layer does not generate light. They offer high contrast in situations with high ambient lighting



Take Quiz 1



ARRL *The national association for*
AMATEUR RADIO

G6A03 - What is the approximate forward threshold voltage of a germanium diode?

- A. 0.1 volt
- B. 0.3 volts
- C. 0.7 volts
- D. 1.0 volts

G6A03 - What is the approximate forward threshold voltage of a germanium diode?

A. 0.1 volt

B. 0.3 volts

C. 0.7 volts

D. 1.0 volts

G6A05 - What is the approximate forward threshold voltage of a silicon junction diode?

- A. 0.1 volt
- B. 0.3 volts
- C. 0.7 volts
- D. 1.0 volts

G6A05 - What is the approximate forward threshold voltage of a silicon junction diode?

- A. 0.1 volt
- B. 0.3 volts
- C. 0.7 volts
- D. 1.0 volts

G6A07 - What are the operating points for a bipolar transistor used as a switch?

- A. Saturation and cutoff
- B. The active region (between cutoff and saturation)
- C. Peak and valley current points
- D. Enhancement and depletion modes

G6A07 - What are the operating points for a bipolar transistor used as a switch?

A. Saturation and cutoff

B. The active region (between cutoff and saturation)

C. Peak and valley current points

D. Enhancement and depletion modes

G6A09 - Which of the following describes MOSFET construction?

- A. The gate is formed by a back-biased junction
- B. The gate is separated from the channel by a thin insulating layer
- C. The source is separated from the drain by a thin insulating layer
- D. The source is formed by depositing metal on silicon

G6A09 - Which of the following describes MOSFET construction?

A. The gate is formed by a back-biased junction

B. The gate is separated from the channel by a thin insulating layer

C. The source is separated from the drain by a thin insulating layer

D. The source is formed by depositing metal on silicon

G6A10 - Which element of a vacuum tube regulates the flow of electrons between cathode and plate?

- A. Control grid
- B. Suppressor grid
- C. Screen grid
- D. Trigger electrode

G6A10 - Which element of a vacuum tube regulates the flow of electrons between cathode and plate?

A. Control grid

B. Suppressor grid

C. Screen grid

D. Trigger electrode

G6A12 - What is the primary purpose of a screen grid in a vacuum tube?

- A. To reduce grid-to-plate capacitance
- B. To increase efficiency
- C. To increase the control grid resistance
- D. To decrease plate resistance

G6A12 - What is the primary purpose of a screen grid in a vacuum tube?

- A. To reduce grid-to-plate capacitance
- B. To increase efficiency
- C. To increase the control grid resistance
- D. To decrease plate resistance

G6B02 - What is meant by the term MMIC?

- A. Multi-Mode Integrated Circuit
- B. Monolithic Microwave Integrated Circuit
- C. Metal Monolayer Integrated Circuit
- D. Mode Modulated Integrated Circuit

G6B02 - What is meant by the term MMIC?

- A. Multi-Mode Integrated Circuit
- B. Monolithic Microwave Integrated Circuit
- C. Metal Monolayer Integrated Circuit
- D. Mode Modulated Integrated Circuit

G6B03 - Which of the following is an advantage of CMOS integrated circuits compared to TTL integrated circuits?

- A. Low power consumption
- B. High power handling capability
- C. Better suited for RF amplification
- D. Better suited for power supply regulation

G6B03 - Which of the following is an advantage of CMOS integrated circuits compared to TTL integrated circuits?

- A. Low power consumption
- B. High power handling capability
- C. Better suited for RF amplification
- D. Better suited for power supply regulation

G6B06 - What kind of device is an integrated circuit operational amplifier?

A. Digital

B. MMIC

C. Programmable Logic

D. Analog

G6B06 - What kind of device is an integrated circuit operational amplifier?

A. Digital

B. MMIC

C. Programmable Logic

D. Analog

G7B03 - Which of the following describes the function of a two-input AND gate?

- A. Output is high when either or both inputs are low
- B. Output is high only when both inputs are high
- C. Output is low when either or both inputs are high
- D. Output is low only when both inputs are high

G7B03 - Which of the following describes the function of a two-input AND gate?

A. Output is high when either or both inputs are low

B. Output is high only when both inputs are high

C. Output is low when either or both inputs are high

D. Output is low only when both inputs are high

G7B05 - How many states does a 3-bit binary counter have?

A. 3

B. 6

C. 8

D. 16

G7B05 - How many states does a 3-bit binary counter have?

A. 3

B. 6

C. 8

D. 16

G7B06 - What is a shift register?

- A. A clocked array of circuits that passes data in steps along the array
- B. An array of operational amplifiers used for tri-state arithmetic operations
- C. A digital mixer
- D. An analog mixer

G7B06 - What is a shift register?

A. A clocked array of circuits that passes data in steps along the array

B. An array of operational amplifiers used for tri-state arithmetic operations

C. A digital mixer

D. An analog mixer

G6B08 - How is an LED biased when emitting light?

- A. In the tunnel-effect region
- B. At the Zener voltage
- C. Reverse biased
- D. Forward biased

G6B08 - How is an LED biased when emitting light?

A. In the tunnel-effect region

B. At the Zener voltage

C. Reverse biased

D. Forward biased

G6B09 (A)

How does a liquid crystal display compare to an LED display?

A. Higher contrast in high ambient lighting

B. Wider dynamic range

C. Higher Power consumption

D. Shorter lifetime

G6B09 (A)

How does a liquid crystal display compare to an LED display?

A. Higher contrast in high ambient lighting

B. Wider dynamic range

C. Higher Power consumption

D. Shorter lifetime

General License Course

Chapter 4.6

Practical Circuits

Rectifiers


- A rectifier diode is an electronic device that converts alternating current (AC, which periodically reverses direction) to direct current (DC, which flows in only one direction). The process is known as rectification.



ARRL The national association for
AMATEUR RADIO

Rectifiers

- Half-wave rectifier - allows current to flow in one-half of the input ac waveform (180°) from the transformer, as shown in "A"
Advantage: only one diode is required
- Full-wave center-trapped rectifier - two half-wave rectifiers operating on alternating half cycles, as shown in "B", using the transformer center tap for the current's return path

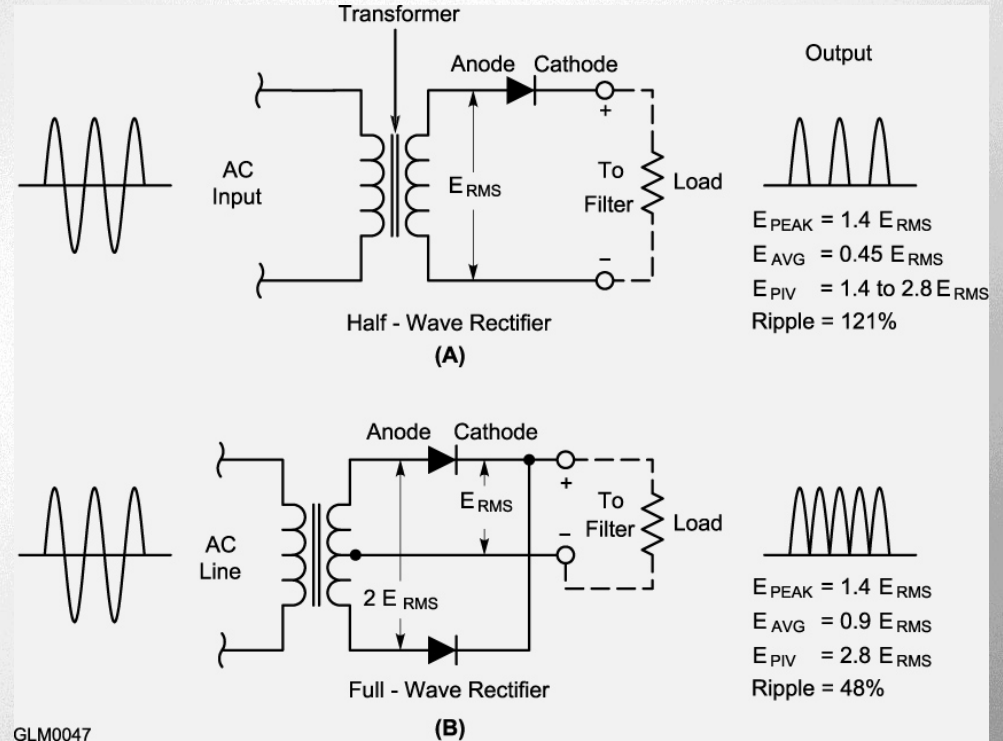

GLM0047




ARRL The national association for
AMATEUR RADIO

Rectifiers

- Full Wave Rectifier Circuits
- Advantage – output is produced during entire 360° of the ac cycle
- Output is a series of pulses at twice the frequency of the input voltage
- Full-wave bridge rectifier – uses a pair of diodes on alternating ac cycle halves




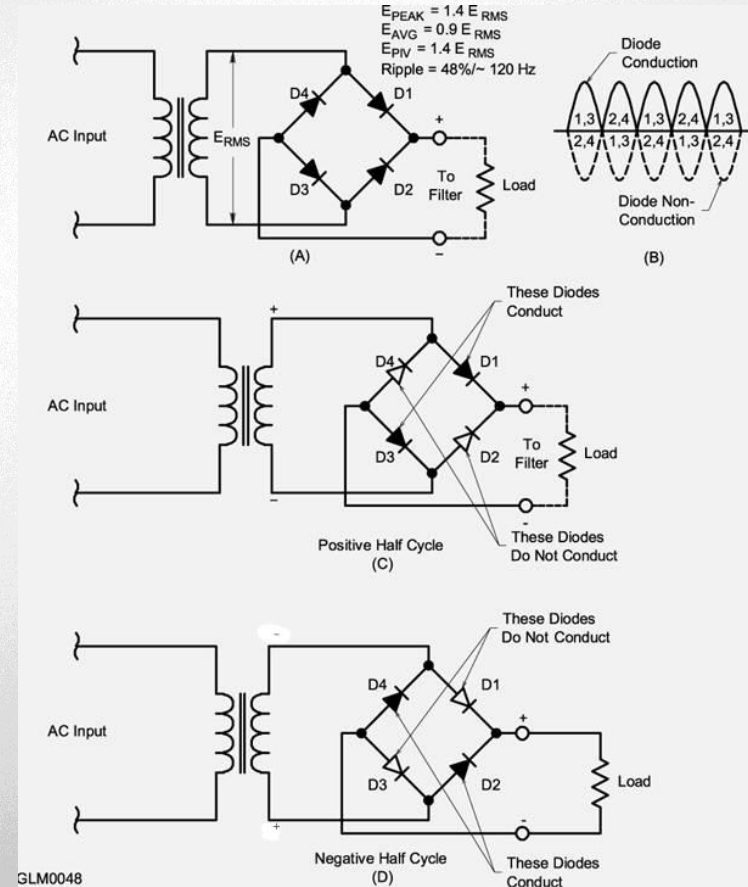ARRL The national association for
AMATEUR RADIO



Filter Circuits

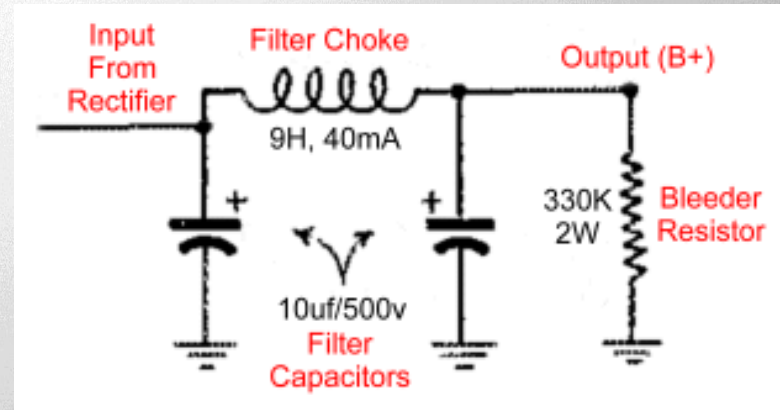
- A Rectifier's *pulsed output* is often unusable as DC
- *Filter networks* – made up of capacitors and inductors
- an inductor to filter (resist) current variations
- a capacitor to filter (resist) voltage variations



Power Supply Filtering



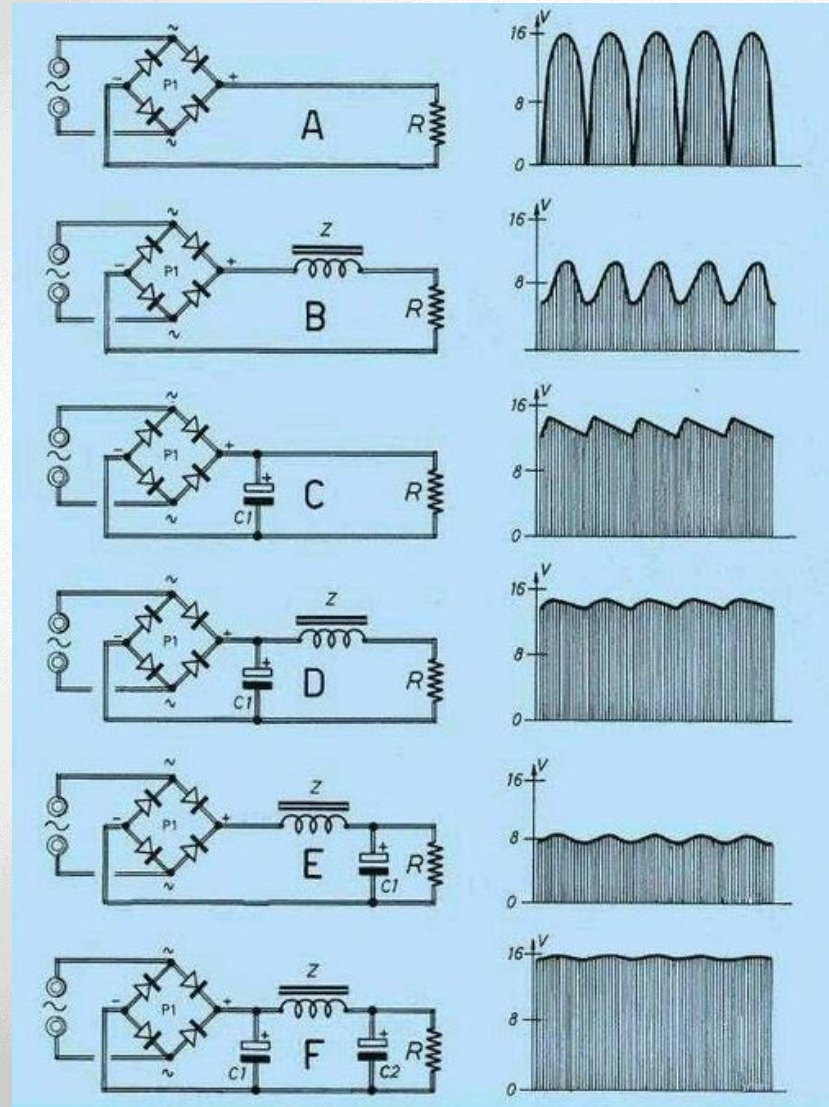
ARRL The national association for
AMATEUR RADIO



Power Supplies

- Power supply safety:
- Fuses (transformer primary side) are used to protect against short circuits or excessive current
- *Bleeder resistors* discharge energy stored in the PS filter capacitors when the supply is turned off

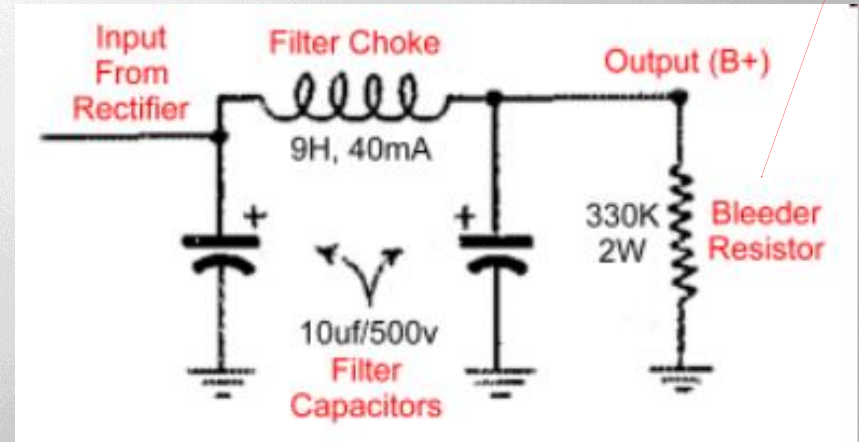Working on power supplies –
wait for the bleeder resistor to
discharge energy, even if the PS
is unplugged



Power Supplies

- **Switching** or Switchmode supplies:
- Transistors switch current pulses at a high frequency (20 kHz or more*) through a transformer then capacitors and inductors filter the voltage
- High frequency operation allows small, lightweight components (transformers, capacitors, inductors) to be used
- **Linear** supplies are very heavy due to their large, iron-core power transformer and large filter inductors/capacitors



ARRL The national association for
AMATEUR RADIO

**RFI suppression must be included in the design.*

Batteries

- Large marine or RV storage batteries are often used as emergency backup power supplies
- Liquid-electrolyte or gel-electrolyte batteries are rated at 12 V but should be maintained at 13.8 V
- Lead-acid batteries are useful until their output drops to 10.5 V
- Discharging batteries past their minimum voltage will reduce the life of the battery



Batteries

- **Never** attempt to recharge a carbon-zinc, alkaline, or silver-nickel type battery (the chemical reaction cannot be reversed)
- Battery self-discharge gradually reduces stored energy over time
- Slow this discharge by storing in a cool, dry place
- Freezing will damage batteries with liquid or gel electrolytes



Rechargeable Batteries

- Different types of rechargeable batteries require different charging methods
- NiCad, NMH, Li-Ion
- Use the *proper type of charger* to maximize the life and usefulness of the battery
- NiCds (or Nicads) – designed to have low internal resistance to supply high discharge current




Alternative Power

- *Solar Power – photovoltaic conversion of sunlight directly to electricity*
- Solar cells are a special type of diode
- The forward voltage created as the electrons cross the P-N junction is approximately 0.5 V dc (open circuit voltage) when fully illuminated
- Individual solar cells can be connected in series to create higher voltages (24 cells to create 12 V) AND in parallel to provide more current.
SERIES-PARALLEL
- *Wind generators use DC generators to charge batteries; an inverter is used to convert to AC, if needed*


Energy Storage

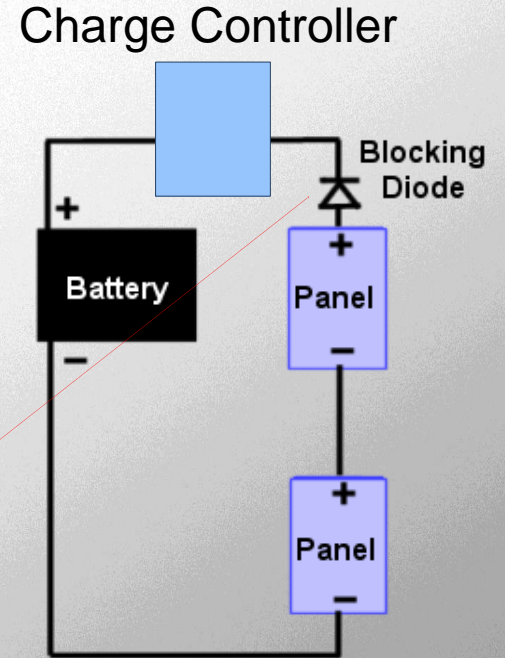- Disadvantage: Wind and solar power require a substantial energy storage system; No wind or sun means no power
- Excess power needs to be stored during peak periods of generation (batteries are the most common method) – a Charge Controller must be included to prevent damage to the batteries
- Diodes (in series) prevent the batteries from discharging back through the solar panels



Audio Connectors

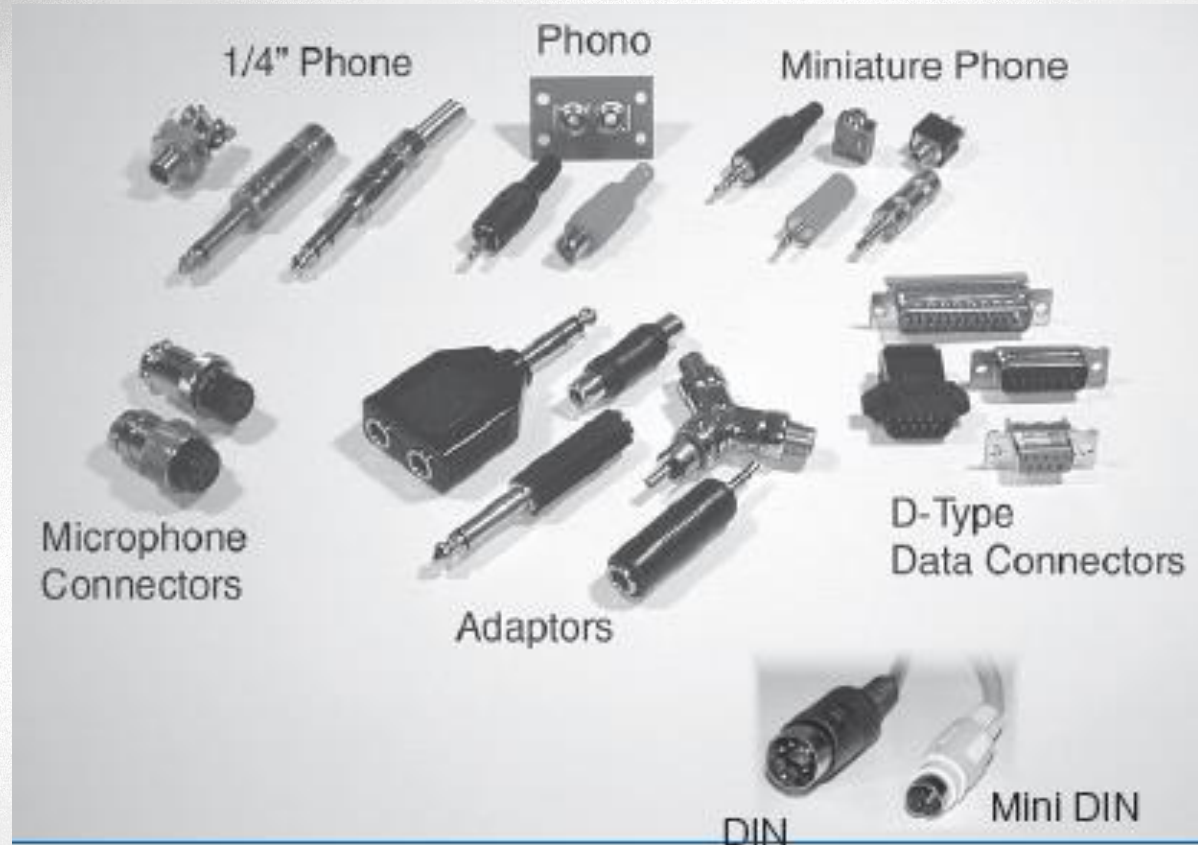- Consumer electronics and Amateur Radio share many of the same connectors




ARRL The national association for
AMATEUR RADIO

Audio Connectors

Phono plugs (also called RCA connectors) are commonly used for low frequency (audio) and DC signals




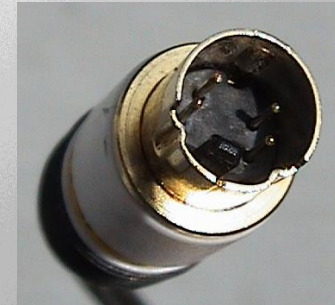DIN or mini-DIN connectors are keyed and have up to 9 pins and are used for audio or control signals for radio equipment



Power Connectors

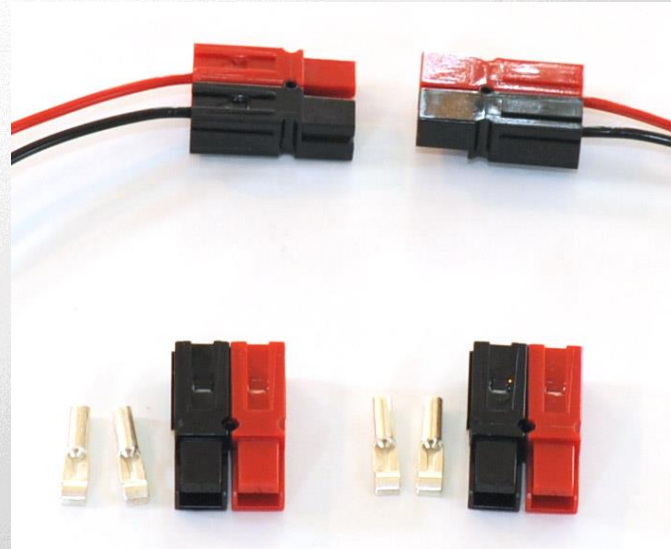Anderson Powerpole connectors have become the standard for connecting radios and associated devices to 12 vdc supplies



ARRL The national association for
AMATEUR RADIO

RF Connectors

Special RF feed line connectors:

“PL-259” (aka UHF) connectors can be used up to 150 MHz

“BNC” connectors can be used up to 4 GHz


“N” connectors are moisture resistant and used up to 10 GHz

“SMA”* connectors are small threaded connectors designed for miniature coaxial cable and are rated up to several GHz



Data Connectors

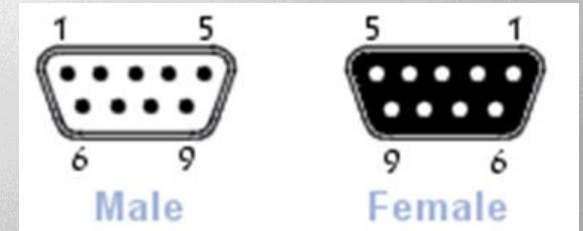- Digital data is exchanged between the computers and radios:
 - *D-type* connectors are used for RS-232 (COM ports) and parallel ports
 - D-type 9-pin connector is referred to as DB-9 or **DE-9** (commonly used for serial ports)
- 25-pin D-type connector used for parallel ports
- *USB* ports are standard for modern computers



Take Quiz 2



ARRL *The national association for*
AMATEUR RADIO

G7A01 - What is the function of a power supply bleeder resistor?

- A. It acts as a fuse for excess voltage
- B. It discharges the filter capacitors when power is removed
- C. It removes shock hazards from the induction coils
- D. It eliminates ground loop current

G7A01 - What is the function of a power supply bleeder resistor?

A. It acts as a fuse for excess voltage

B. It discharges the filter capacitors when power is removed

C. It removes shock hazards from the induction coils

D. It eliminates ground loop current

G7A02 - Which of the following components are used in a power supply filter network?

- A. Diodes
- B. Transformers and transducers
- C. Capacitors and inductors
- D. All these choices are correct

G7A02 - Which of the following components are used in a power supply filter network?

A. Diodes

B. Transformers and transducers

C. Capacitors and inductors

D. All these choices are correct

G7A03 - Which type of rectifier circuit uses two diodes and a center-tapped transformer?

- A. Full-wave
- B. Full-wave bridge
- C. Half-wave
- D. Synchronous

G7A03 - Which type of rectifier circuit uses two diodes and a center-tapped transformer?

A. Full-wave

B. Full-wave bridge

C. Half-wave

D. Synchronous



ARRL The national association for
AMATEUR RADIO

G7A04 - What is characteristic of a half-wave rectifier in a power supply?

- A. Only one diode is required
- B. The ripple frequency is twice that of a full-wave rectifier
- C. More current can be drawn from the half-wave rectifier
- D. The output voltage is two times the peak input voltage

G7A04 - What is characteristic of a half-wave rectifier in a power supply?

A. Only one diode is required

B. The ripple frequency is twice that of a full-wave rectifier

C. More current can be drawn from the half-wave rectifier

D. The output voltage is two times the peak input voltage

G7A05 - What portion of the AC cycle is converted to DC by a half-wave rectifier?

- A. 90 degrees
- B. 180 degrees
- C. 270 degrees
- D. 360 degrees

G7A05 - What portion of the AC cycle is converted to DC by a half-wave rectifier?

A. 90 degrees

B. 180 degrees

C. 270 degrees

D. 360 degrees



ARRL

The national association for
AMATEUR RADIO

G7A06 - What portion of the AC cycle is converted to DC by a full-wave rectifier?

- A. 90 degrees
- B. 180 degrees
- C. 270 degrees
- D. 360 degrees

G7A06 - What portion of the AC cycle is converted to DC by a full-wave rectifier?

- A. 90 degrees
- B. 180 degrees
- C. 270 degrees
- D. 360 degrees



ARRL The national association for
AMATEUR RADIO

G7A07 - What is the output waveform of an unfiltered full-wave rectifier connected to a resistive load?

- A. A series of DC pulses at twice the frequency of the AC input
- B. A series of DC pulses at the same frequency as the AC input
- C. A sine wave at half the frequency of the AC input
- D. A steady DC voltage

G7A07 - What is the output waveform of an unfiltered full-wave rectifier connected to a resistive load?

- A. A series of DC pulses at twice the frequency of the AC input
- B. A series of DC pulses at the same frequency as the AC input
- C. A sine wave at half the frequency of the AC input
- D. A steady DC voltage

G7A08 - Which of the following is characteristic of a switchmode power supply as compared to a linear power supply?

- A. Faster switching time makes higher output voltage possible
- B. Fewer circuit components are required
- C. High-frequency operation allows the use of smaller components
- D. Inherently more stable

G7A08 - Which of the following is characteristic of a switchmode power supply as compared to a linear power supply?

- A. Faster switching time makes higher output voltage possible
- B. Fewer circuit components are required
- C. High-frequency operation allows the use of smaller components
- D. Inherently more stable

G4E08 - In what configuration are the individual cells in a solar panel connected together?

- A. Series-parallel
- B. Shunt
- C. Bypass
- D. Full-wave bridge

G4E08 - In what configuration are the individual cells in a solar panel connected together?

A. Series-parallel

B. Shunt

C. Bypass

D. Full-wave bridge

G4E09 - What is the approximate open-circuit voltage from a fully illuminated silicon photovoltaic cell?

A. 0.02 VDC

B. 0.5 VDC

C. 0.2 VDC

D. 1.38 VDC



ARRL *The national association for*
AMATEUR RADIO

G4E09 - What is the approximate open-circuit voltage from a fully illuminated silicon photovoltaic cell?

A. 0.02 VDC

B. 0.5 VDC

C. 0.2 VDC

D. 1.38 VDC

G4E10 - Why should a series diode be connected between a solar panel and a storage battery that is being charged by the panel?

- A. To prevent overload by regulating the charging voltage
- B. To prevent discharge of the battery through the panel during times of low or no illumination
- C. To limit the current flowing from the panel to a safe value
- D. To prevent damage to the battery due to excessive voltage at high illumination levels

G4E10 - Why should a series diode be connected between a solar panel and a storage battery that is being charged by the panel?

A. To prevent overload by regulating the charging voltage

B. To prevent discharge of the battery through the panel during times of low or no illumination

C. To limit the current flowing from the panel to a safe value

D. To prevent damage to the battery due to excessive voltage at high illumination levels

G4E11 - What precaution should be taken when connecting a solar panel to a lithium iron phosphate battery?

- A. Ground the solar panel outer metal framework
- B. Ensure the battery is placed terminals-up
- C. A series resistor must be in place
- D. The solar panel must have a charge controller

G4E11 - What precaution should be taken when connecting a solar panel to a lithium iron phosphate battery?

- A. Ground the solar panel outer metal framework
- B. Ensure the battery is placed terminals-up
- C. A series resistor must be in place
- D. The solar panel must have a charge controller

G6A01 - What is the minimum allowable discharge voltage for maximum life of a standard 12-volt lead-acid battery?

A. 6 volts

B. 8.5 volts

C. 10.5 volts

D. 12 volts

G6A01 - What is the minimum allowable discharge voltage for maximum life of a standard 12-volt lead-acid battery?

A. 6 volts

B. 8.5 volts

C. 10.5 volts

D. 12 volts

G6A02 - What is an advantage of batteries with low internal resistance?

- A. Long life
- B. High discharge current
- C. High voltage
- D. Rapid recharge

G6A02 - What is an advantage of batteries with low internal resistance?

A. Long life

B. High discharge current

C. High voltage

D. Rapid recharge

G6B04 - What is a typical upper frequency limit for low SWR operation of 50-ohm BNC connectors?

- A. 50 MHz
- B. 500 MHz
- C. 4 GHz
- D. 40 GHz

G6B04 - What is a typical upper frequency limit for low SWR operation of 50-ohm BNC connectors?

A. 50 MHz

B. 500 MHz

C. 4 GHz

D. 40 GHz



ARRL *The national association for*
AMATEUR RADIO

G6B07 - Which of the following describes a type N connector?

- A. A moisture-resistant RF connector useful to 10 GHz
- B. A small bayonet connector used for data circuits
- C. A low noise figure VHF connector
- D. A nickel plated version of the PL-259

G6B07 - Which of the following describes a type N connector?

A. A moisture-resistant RF connector useful to 10 GHz

B. A small bayonet connector used for data circuits

C. A low noise figure VHF connector

D. A nickel plated version of the PL-259

G6B11 - What is an SMA connector?

- A. A type-S to type-M adaptor
- B. A small threaded connector suitable for signals up to several GHz
- C. A connector designed for serial multiple access signals
- D. A type of push-on connector intended for high-voltage applications

G6B11 - What is an SMA connector?

A. A type-S to type-M adaptor

B. A small threaded connector suitable for signals up to several GHz

C. A connector designed for serial multiple access signals

D. A type of push-on connector intended for high-voltage applications

G6B12 - Which of these connector types is commonly used for low frequency or dc signal connections to a transceiver?

A. PL-259

B. BNC

C. RCA Phono

D. Type N

G6B12 - Which of these connector types is commonly used for low frequency or dc signal connections to a transceiver?

A. PL-259

B. BNC

C. RCA Phono

D. Type N

General License Course

Chapter 4.7

Basic Test Equipment

Analog Meters

- A Volt-ohm meter (VOM) is the most basic piece of test equipment
- Measures – volts, current, resistance
- Tests – continuity, diodes, transistors
- Analog Meters
- Analog meters have a moving needle and calibrated scales on the meter face
- Analog meters are useful for finding a maximum or minimum reading, such as when adjusting a tuned circuit



Digital Meters

- Digital meters (DMMs) offer significantly greater precision than analog meters
- Digital meters often have useful features:
 - *auto-ranging* to automatically select the proper display range
 - *peak hold* to capture maximum values
- When measuring voltage, the meter should have a high input impedance to place the minimum load on the circuit being measured



ARRL The national association for
AMATEUR RADIO

Loading Effect of a Voltmeter

- High resistance circuits are susceptible to **Voltmeter loading**.

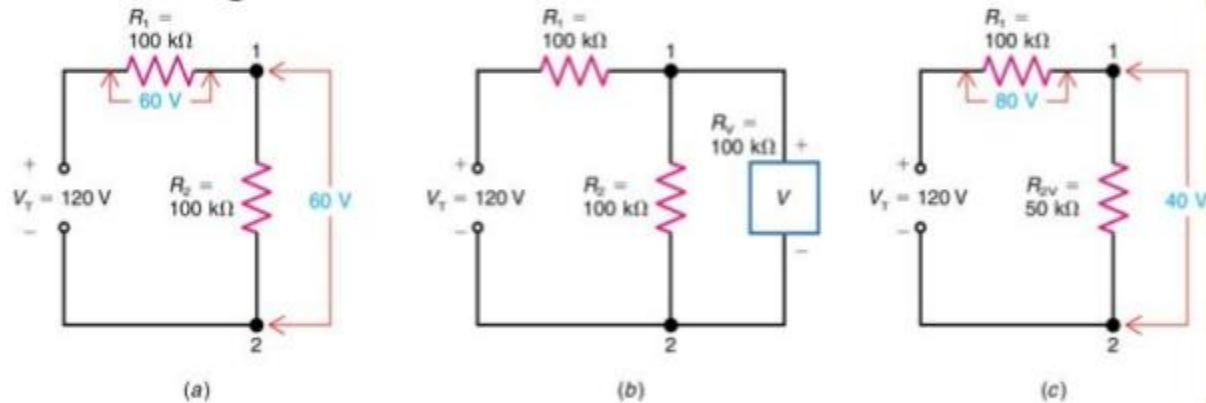


Fig. 8-8: How loading effect of the voltmeter can reduce the voltage reading. (a) High-resistance series circuit without voltmeter. (b) Connecting voltmeter across one of the series resistances. (c) Reduced R and V between points 1 and 2 caused by the voltmeter as a parallel branch across R_2 . The R_{2V} is the equivalent of R_2 and R_V in parallel.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



ARRL The national association for
AMATEUR RADIO


Oscilloscope

- The oscilloscope (O-scope) provides a visual display of **voltage vs. time**
- Updated rapidly enough to give a real-time picture of the signal
- **Fast-changing complex waveforms can be measured**
- **External signals are connected to horizontal and vertical channel amplifier inputs to control the display**
- Variable gain and update rates are available to display many types of signals.



Oscilloscope

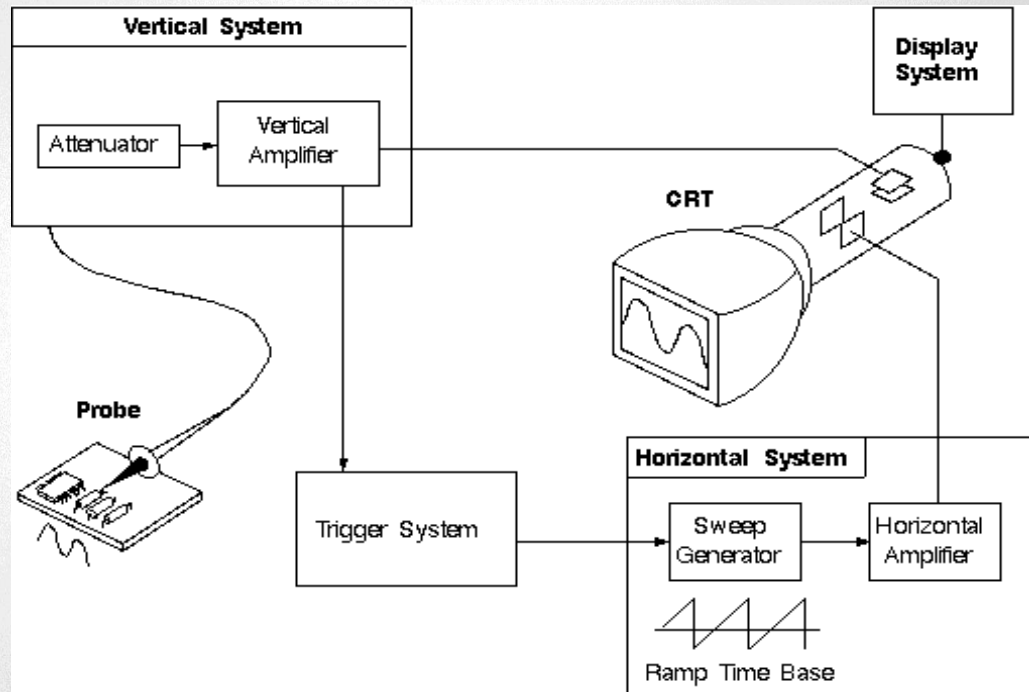An oscilloscope is an item of test equipment that contains horizontal and vertical channel amplifiers



ARRL The national association for
AMATEUR RADIO

Oscilloscope

<C:\Users\ai2n\Videos\General Course - Videos\O-Scope Time Base Demo.wmv>



ARRL *The national association for*
AMATEUR RADIO

Monitoring Oscilloscope


- The transmitter's attenuated RF output connects to the vertical channel of the oscilloscope to monitor the signal
- Monitoring helps adjust CW keying waveforms, mic gain, and speech processing
- The scope shows the effects of any adjustments that might cause distortion
- A “scope” provides information that numeric meters can't measure.



ARRL The national association for
AMATEUR RADIO

Impedance & Resonance Measurement

- *An antenna analyzer* contains a signal generator, frequency counter, SWR bridge, and impedance meter
- Connects to the antenna and feed line to measure **Standing Wave Ratio (SWR)** using very small signals for measurements
- Impedance measurements show resonance
- Measures feed line/coax velocity factor, electrical length, and characteristic impedance
- Can be negatively affected by strong nearby signals

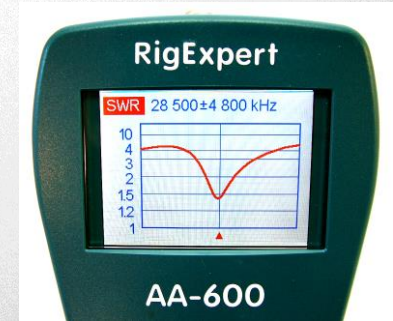

ARRL The national association for
AMATEUR RADIO

Field Strength & Power Meters

- Field strength meters measure the electrical field of transmitted signals
- Field strength meters can be used during antenna and transmitter adjustments
- Field strength meters can be used to measure antenna radiation patterns
- Standing Wave Ratio (SWR) can be determined from forward and reflected power measurements made with a *directional wattmeter*



ARRL The national association for
AMATEUR RADIO

Field Strength Meter

[C:\Users\ai2n\Videos\General Course -
Videos\Field Strength Meter Demo.wmv](C:\Users\ai2n\Videos\General Course - Videos\Field Strength Meter Demo.wmv)



ARRL *The national association for*
AMATEUR RADIO

Take Quiz 3



ARRL *The national association for*
AMATEUR RADIO

G4B01 - What item of test equipment contains horizontal and vertical channel amplifiers?

- A. An ohmmeter
- B. A signal generator
- C. An ammeter
- D. An oscilloscope

G4B01 - What item of test equipment contains horizontal and vertical channel amplifiers?

A. An ohmmeter

B. A signal generator

C. An ammeter

D. An oscilloscope

G4B02 - Which of the following is an advantage of an oscilloscope versus a digital voltmeter?

- A. An oscilloscope uses less power
- B. Complex impedances can be easily measured
- C. Greater precision
- D. Complex waveforms can be measured

G4B02 - Which of the following is an advantage of an oscilloscope versus a digital voltmeter?

- A. An oscilloscope uses less power
- B. Complex impedances can be easily measured
- C. Greater precision
- D. Complex waveforms can be measured

G4B03 - Which of the following is the best instrument to use for checking the keying waveform of a CW transmitter?

- A. An oscilloscope
- B. A field strength meter
- C. A sidetone monitor
- D. A wavemeter

G4B03 - Which of the following is the best instrument to use for checking the keying waveform of a CW transmitter?

A. An oscilloscope

B. A field strength meter

C. A sidetone monitor

D. A wavemeter

G4B04 - What signal source is connected to the vertical input of an oscilloscope when checking the RF envelope pattern of a transmitted signal?

- A. The local oscillator of the transmitter
- B. An external RF oscillator
- C. The transmitter balanced mixer output
- D. The attenuated RF output of the transmitter

G4B04 - What signal source is connected to the vertical input of an oscilloscope when checking the RF envelope pattern of a transmitted signal?

- A. The local oscillator of the transmitter
- B. An external RF oscillator
- C. The transmitter balanced mixer output
- D. The attenuated RF output of the transmitter

G4B05 - Why do voltmeters have high input impedance?

- A. It improves the frequency response
- B. It allows for higher voltages to be safely measured
- C. It improves the resolution of the readings
- D. It decreases the loading on circuits being measured

G4B05 - Why do voltmeters have high input impedance?

- A. It improves the frequency response
- B. It allows for higher voltages to be safely measured
- C. It improves the resolution of the readings
- D. It decreases the loading on circuits being measured

G4B06 - What is an advantage of a digital multimeter as compared to an analog multimeter?

- A. Better for measuring computer circuits
- B. Less prone to overload
- C. Higher precision
- D. Faster response

G4B06 - What is an advantage of a digital multimeter as compared to an analog multimeter?

A. Better for measuring computer circuits

B. Less prone to overload

C. Higher precision

D. Faster response

G4B09 - When is an analog multimeter preferred to a digital multimeter?

- A. When testing logic circuits
- B. When high precision is desired
- C. When measuring the frequency of an oscillator
- D. When adjusting circuits for maximum or minimum values

G4B09 - When is an analog multimeter preferred to a digital multimeter?

- A. When testing logic circuits
- B. When high precision is desired
- C. When measuring the frequency of an oscillator
- D. When adjusting circuits for maximum or minimum values

G4B10 - Which of the following can be determined with a directional wattmeter?

- A. Standing wave ratio
- B. Antenna front-to-back ratio
- C. RF interference
- D. Radio wave propagation

G4B10 - Which of the following can be determined with a directional wattmeter?

A. Standing wave ratio

B. Antenna front-to-back ratio

C. RF interference

D. Radio wave propagation

G4B11 - Which of the following must be connected to an antenna analyzer when it is being used for SWR measurements?

- A. Receiver
- B. Transmitter
- C. Antenna and feed line
- D. All these choices are correct

G4B11 - Which of the following must be connected to an antenna analyzer when it is being used for SWR measurements?

A. Receiver

B. Transmitter

C. Antenna and feed line

D. All these choices are correct

G4B12 - What effect can strong signals from nearby transmitters have on an antenna analyzer?

- A. Desensitization which can cause intermodulation products which interfere with impedance readings
- B. Received power that interferes with SWR readings
- C. Generation of harmonics which interfere with frequency readings
- D. All these choices are correct

G4B12 - What effect can strong signals from nearby transmitters have on an antenna analyzer?

A. Desensitization which can cause intermodulation products which interfere with impedance readings

B. Received power that interferes with SWR readings

C. Generation of harmonics which interfere with frequency readings

D. All these choices are correct

G4B13 - Which of the following can be measured with an antenna analyzer?

- A. Front-to-back ratio of an antenna
- B. Power output from a transmitter
- C. Impedance of coaxial cable
- D. Gain of a directional antenna

G4B13 - Which of the following can be measured with an antenna analyzer?

A. Front-to-back ratio of an antenna

B. Power output from a transmitter

C. Impedance of coaxial cable

D. Gain of a directional antenna

Next Week

Chapters 5.1 – 5.4